

EIE2050

Digital Logic and Systems

Professor Qijun Zhang

Office: Room 404, Research A Building

Latches and Flip-Flops

- Latches
- Flip-flops
- Applications

Reading material: Chapter 7 of Textbook:

Textbook: *Digital Fundamentals (global edition, 11th edition)*, by Thomas Floyd, Pearson 2015.


The examples used in the lecture are based on the textbook.

Latches and Flip-Flops


- Latches
 - S-R latch
 - Gated S-R latch
 - Gated D latch

Latches and Flip-Flops

 - S-R Latch (set-reset latch): Logic diagram




Active-HIGH input S-R latch

 


Active-LOW input \bar{S} - \bar{R} latch

Latches and Flip-Flops


- S-R Latch: Logic symbols

 

Active-HIGH input
S-R latch

 

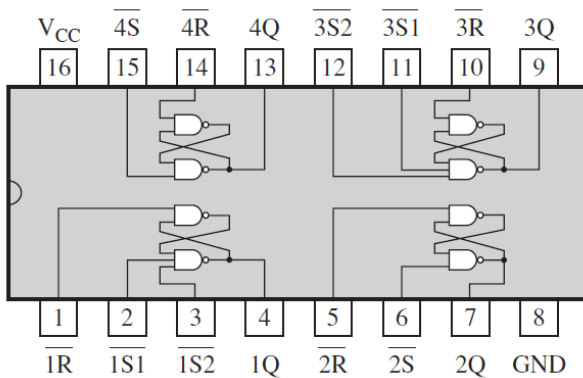Active-LOW input
 \bar{S} - \bar{R} latch





74HC279A, a quad \bar{S} - \bar{R} latch

Truth table for an active-LOW input \bar{S} - \bar{R} latch.

Inputs		Outputs		Comments
\bar{S}	\bar{R}	Q	\bar{Q}	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition


Latches and Flip-Flops

  - Active LOW \bar{S} - \bar{R} Latch: waveform analysis




Latches and Flip-Flops

- Gated S-R Latch

 


Logic diagram

 


Logic symbol

Waveform analysis

 


Latches and Flip-Flops

- Gated D Latch

 


Logic diagram

 

Logic symbol


Waveform analysis

 


Latches and Flip-Flops

- Edge triggered Flip-Flops
 - D Flip-flop
 - J-K Flip-flop

positive edge-triggered

 

negative edge-triggered

 


D Flip-flop


J-K Flip-flop

Latches and Flip-Flops

- D Flip-Flops

 

D=1 (SET)

 


D=0 (RESET)

Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
D	CLK	Q	\bar{Q}	
0	↑	0	1	RESET
1	↑	1	0	SET


↑ = clock transition LOW to HIGH

 

Waveform analysis

Latches and Flip-Flops

- J-K Flip-Flops
(J-K: Jack Kilby)

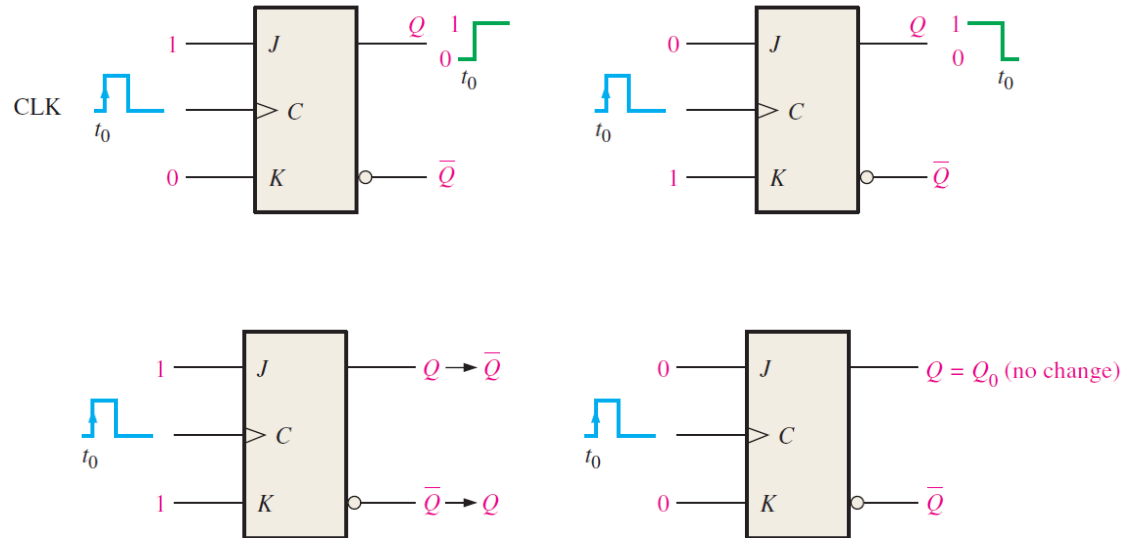

Truth table for a positive edge-triggered J-K flip-flop.


Inputs			Outputs		Comments
J	K	CLK	Q	\bar{Q}	
0	0	\uparrow	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	\bar{Q}_0	Q_0	Toggle

\uparrow = clock transition LOW to HIGH


Q_0 = output level prior to clock transition

Latches and Flip-Flops

- J-K Flip-Flops


 


Waveform analysis

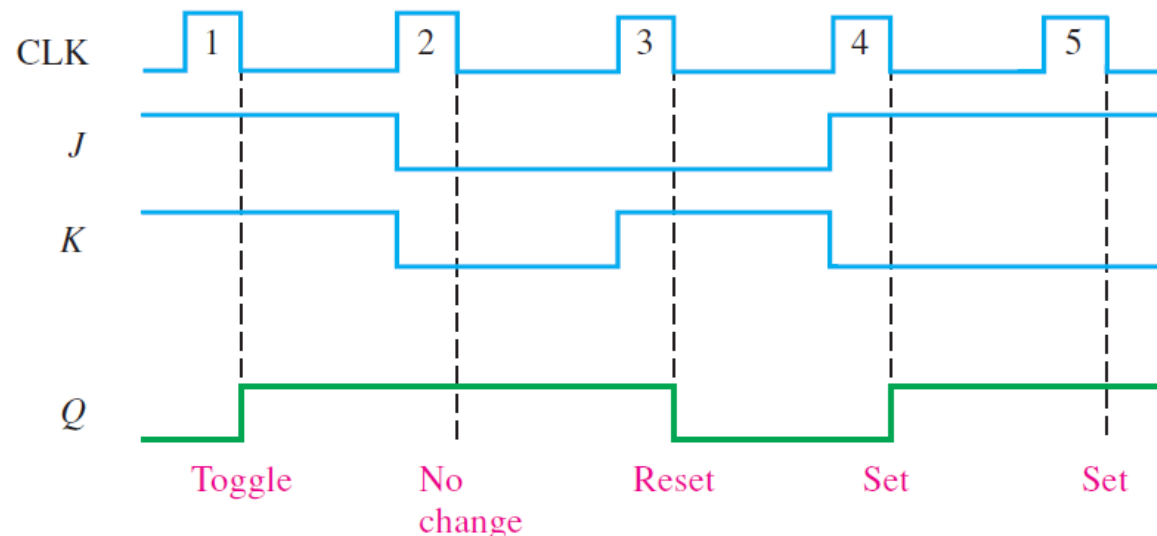

Latches and Flip-Flops

- Edge-Triggered Operation: D Flip-Flops

 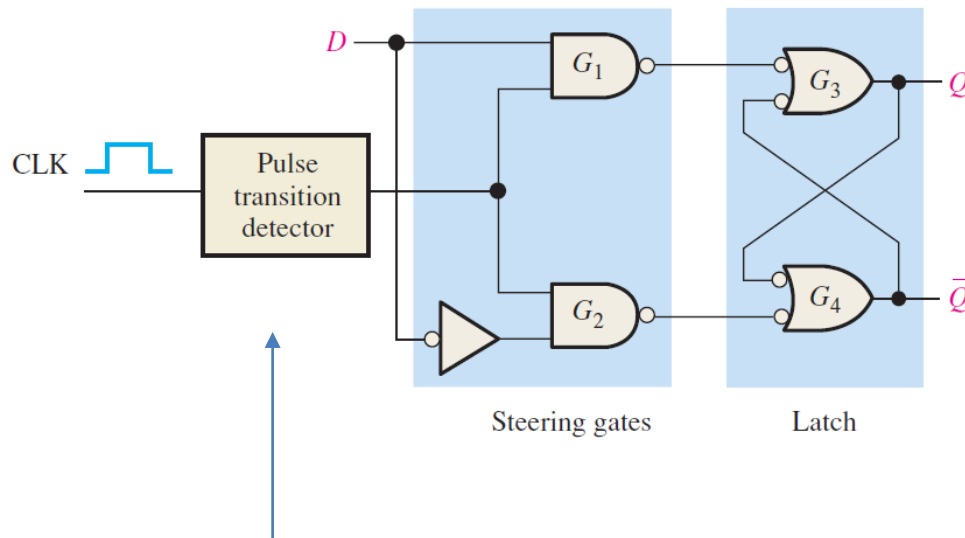


Pulse transition detector


Because the triggering effect by this short pulse (spike), D needs to maintain its intended value only for a short duration.

Latches and Flip-Flops

 - Edge-Triggered Operation: J-K Flip-Flops




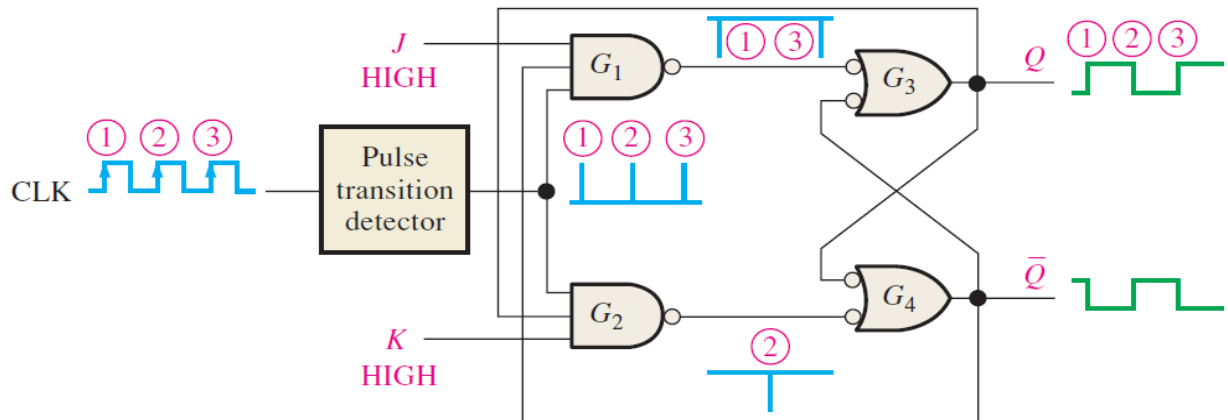Operation
Example:
 $J=K=1$,
 Q and \bar{Q} toggles




Latches and Flip-Flops

 - D Flip-Flop with Active-LOW Preset and Clear Inputs



Logic symbol

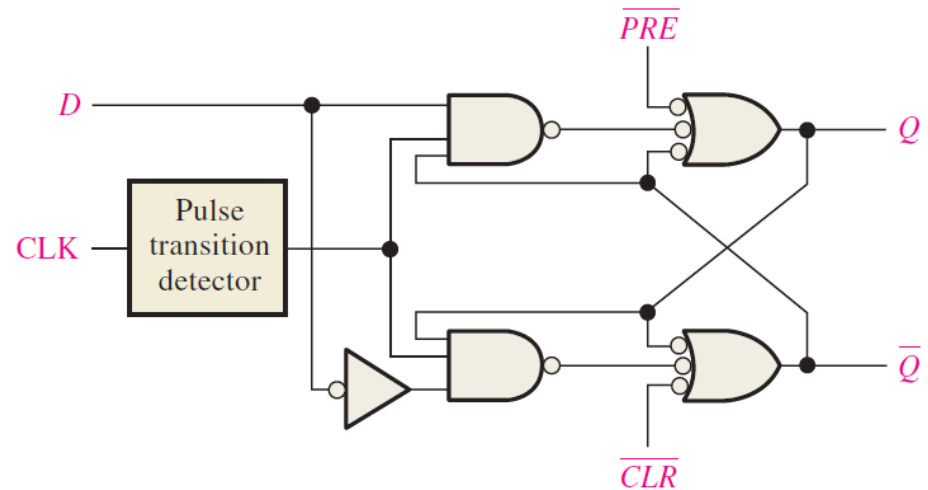


logic diagram

Synchronous inputs: D
Asynchronous inputs: PRE, CLR


PRE: to set $Q=1$
CLR: to set $Q=0$

Latches and Flip-Flops

 - D Flip-Flop with Active-LOW Preset and Clear Inputs




Logic symbol

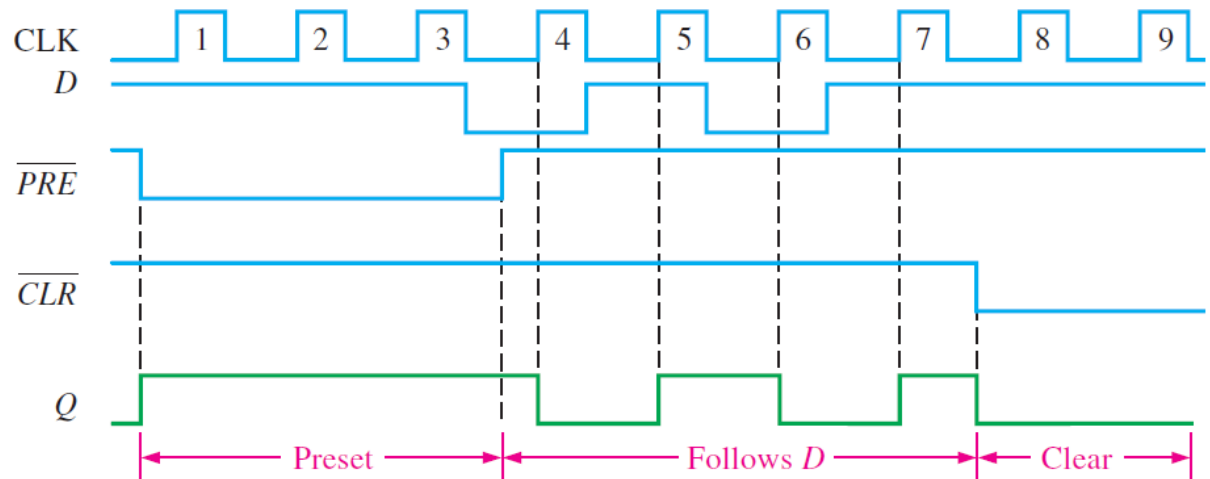

Waveform analysis

Latches and Flip-Flops


- Flip-flops in 74 Series

 

74HC74

Dual

positive edge-triggered
D flip-flops

 



74HC112

Dual

negative edge-triggered
J-K flip-flops

Latches and Flip-Flops

- J-K Flip-flop Example

  

Waveform analysis

74HC112
Dual
negative edge-triggered
J-K flip-flops



Synchronous inputs: J, K
Asynchronous inputs: PRE, CLR

Latches and Flip-Flops



- Flip-Flop Operating Characteristics

Propagation Delays:



Clock to output

  

PRE/CLR to output

  

Setup time, hold time

  

Latches and Flip-Flops

- Flip-Flop Operating Characteristics: example

Comparison of operating parameters for four IC families of flip-flops of the same type at 25°C.


Parameter	CMOS		Bipolar (TTL)	
	74HC74A	74AHC74	74LS74A	74F74
t_{PHL} (CLK to Q)	17 ns	4.6 ns	40 ns	6.8 ns
t_{PLH} (CLK to Q)	17 ns	4.6 ns	25 ns	8.0 ns
$t_{PHL}(\overline{CLR}$ to Q)	18 ns	4.8 ns	40 ns	9.0 ns
$t_{PLH}(\overline{PRE}$ to Q)	18 ns	4.8 ns	25 ns	6.1 ns
t_s (set-up time)	14 ns	5.0 ns	20 ns	2.0 ns
t_h (hold time)	3.0 ns	0.5 ns	5 ns	1.0 ns
t_W (CLK HIGH)	10 ns	5.0 ns	25 ns	4.0 ns
t_W (CLK LOW)	10 ns	5.0 ns	25 ns	5.0 ns
$t_W(\overline{CLR}/\overline{PRE})$	10 ns	5.0 ns	25 ns	4.0 ns
f_{max}	35 MHz	170 MHz	25 MHz	100 MHz
Power, quiescent	0.012 mW	1.1 mW		
Power, 50% duty cycle			44 mW	88 mW

Latches and Flip-Flops


- Flip-Flop Application Examples
 - Parallel data storage
 - Frequency division
 - Counting
 - 555 timer as astable multivibrator

Latches and Flip-Flops

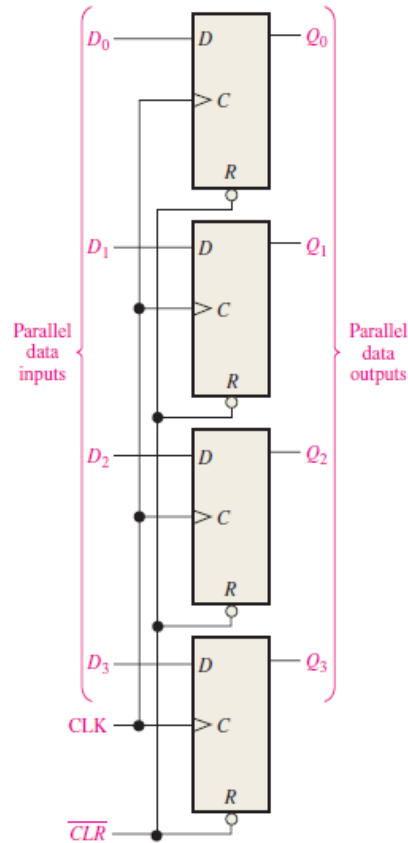- Flip-Flop Application Examples – parallel data storage





A 4-bit register for data storage

 



Waveform analysis

Latches and Flip-Flops

  - Flip-Flop Application Examples – frequency division



Divide the frequency by 2

  


Divide the frequency by 4


Latches and Flip-Flops

- Flip-Flop Application Examples – counting

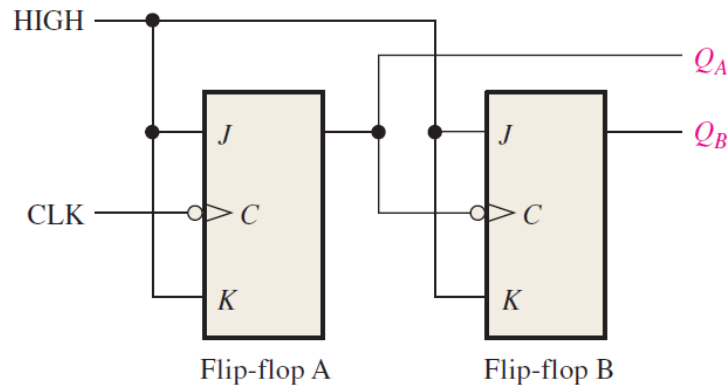J-K flip-flops used to generate a binary counting sequence (00, 01, 10, 11)




To count the number of pulses in CLK

 


Latches and Flip-Flops

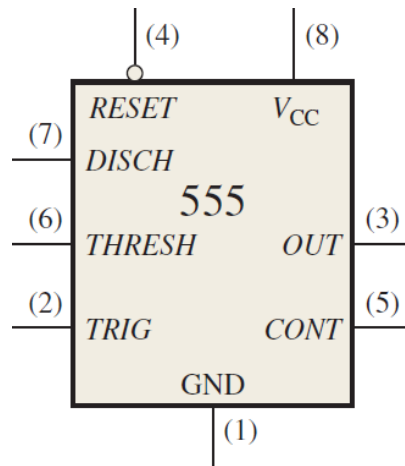- Flip-Flop Application Examples – 555 timer





555 timer external view

 

Internal view of 555 timer

Latches and Flip-Flops

 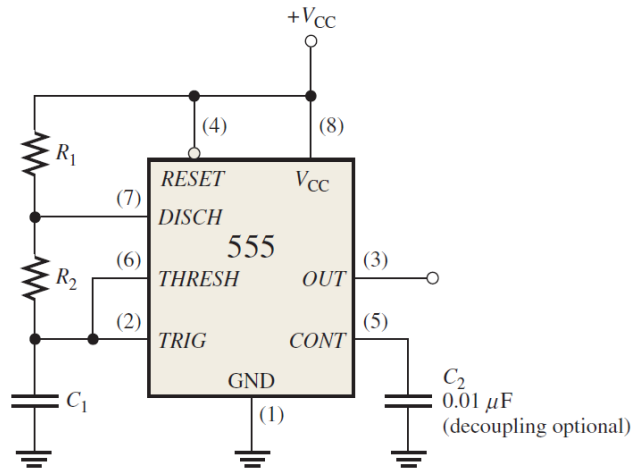- Flip-Flop Application Example
 - 555 timer connected as an astable multivibrator (oscillator)



$$\text{frequency of the pulses} = \frac{1.44}{(R_1 + 2R_2)C_1}$$