

EIE2050 Assignment 2

Answer the questions and submit hardcopies to TC fifth floor **before 5:30pm, 24th October**.

Note: 1. There are four assignments in the course, totally having 25% weight in final evaluation.

2. A mark of zero will be given if plagiarism is found.

1. Apply *DeMorgan's theorems* to each expression:

(a) $\overline{AB(\overline{C} + D)}$ (b) $\overline{AB(\overline{CD} + EF)}$ (c) $\overline{(A + B + \overline{C} + D)} + \overline{ABCD}$

(d) $\overline{(A + B + \overline{C} + D)} \overline{(ABCD)}$ (e) $\overline{AB(\overline{CD} + EF)(\overline{AB} + \overline{CD})}$

2. Construct a truth table for each of the following Boolean expression:

(a) $A+B+C$ (b) ABC (c) $AB+BC+CA$

(d) $(A+B)(B+C)(C+A)$ (e) $A\overline{B} + B\overline{C} + C\overline{A}$

3. Convert the following expressions to sum-of-product (SOP) forms:

(a) $BC+DE(BC+DE)$ (b) $BC(\overline{CD} + CE)$ (c) $B + C[BD + (C + \overline{D})E]$

4. Use a Karnaugh map to reduce each expression to a minimum SOP form:

(a) $A+BC+CD$ (b) $\overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + ABCD + ABC\overline{D}$

(c) $(\overline{A}\overline{B} + A\overline{B})(CD + C\overline{D})$ (d) $\overline{A}\overline{B} + A\overline{B} + \overline{C}\overline{D} + C\overline{D}$

(e) $\overline{A}B(\overline{C}\overline{D} + \overline{C}D) + AB(\overline{C}\overline{D} + \overline{C}D) + \overline{A}\overline{B}\overline{C}D$



5. Use a Karnaugh map to find the minimum POS for each expression:

(a) $(A + B + C)(\overline{A} + \overline{B} + \overline{C})(A + B + \overline{C})$

(b) $(A + \overline{B})(\overline{A} + C)(A + \overline{B} + \overline{C})(\overline{A} + \overline{B} + C)$

(c) $A(B + \overline{C})(\overline{A} + C)(A + \overline{B} + C)(\overline{A} + B + \overline{C})$

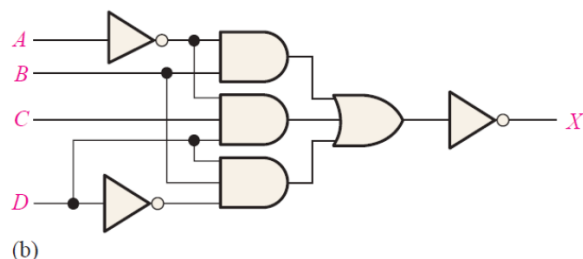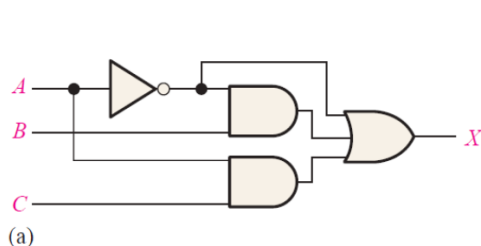6. Write the output expression for each circuit below.



7. Use NAND gates, NOR gates, or combinations of both to implement the following logic expressions as stated:

(a) $X = AB + CD + \overline{A} + \overline{B}(AD + \overline{B}E)$

(b) $X = A\overline{B}C\overline{D} + D\overline{E}F + \overline{A}F$

(c) $X = \overline{A}[B + \overline{C}(\overline{D} + E)]$

8. Implement a logic circuit for the truth table below.

TABLE 5-9

Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>X</i>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

9. Using NAND gates only to implement the following expressions.

(a) $X = A + B + C$

(b) $X = ABC$

(c) $X = A\bar{B} + \bar{A}B$

(d) $X = AB + CD$

10. Using NOR gates only to implement the following expressions.

(a) $X = ABC$

(b) $X = A + B$

(c) $X = A + B + \bar{C}$

(d) $X = \bar{A}\bar{B} + \bar{C}\bar{D}$

(e) $X = A\bar{B} + \bar{A}B$

(f) $X = (A + B)(C + \bar{D})$

(g) $X = AB[C(\bar{D}\bar{E} + \bar{A}\bar{B}) + \bar{B}\bar{C}\bar{E}]$