

EIE2050

Digital Logic and Systems



Professor Qijun Zhang

Office: Room 404, Research A Building

VHDL Basics

- Programmable Logic Devices
- VHDL

7-Segment Display Example

  

Segment a: 0, 2, 3, 5, 6, 7, 8, 9

b: 0, 1, 2, 3, 4, 7, 8, 9

Standard SOP:

$$X_a = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D}$$

$$X_b = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$$







Minimum SOP:

$$X_a = A + C + BD + \bar{B}\bar{D}$$

$$X_b = \bar{B} + CD + \bar{C}\bar{D}$$


Fixed Function Logic Gates

- They are non-programmable:

      

Programmable Logic Devices


- Programmable Array Logic

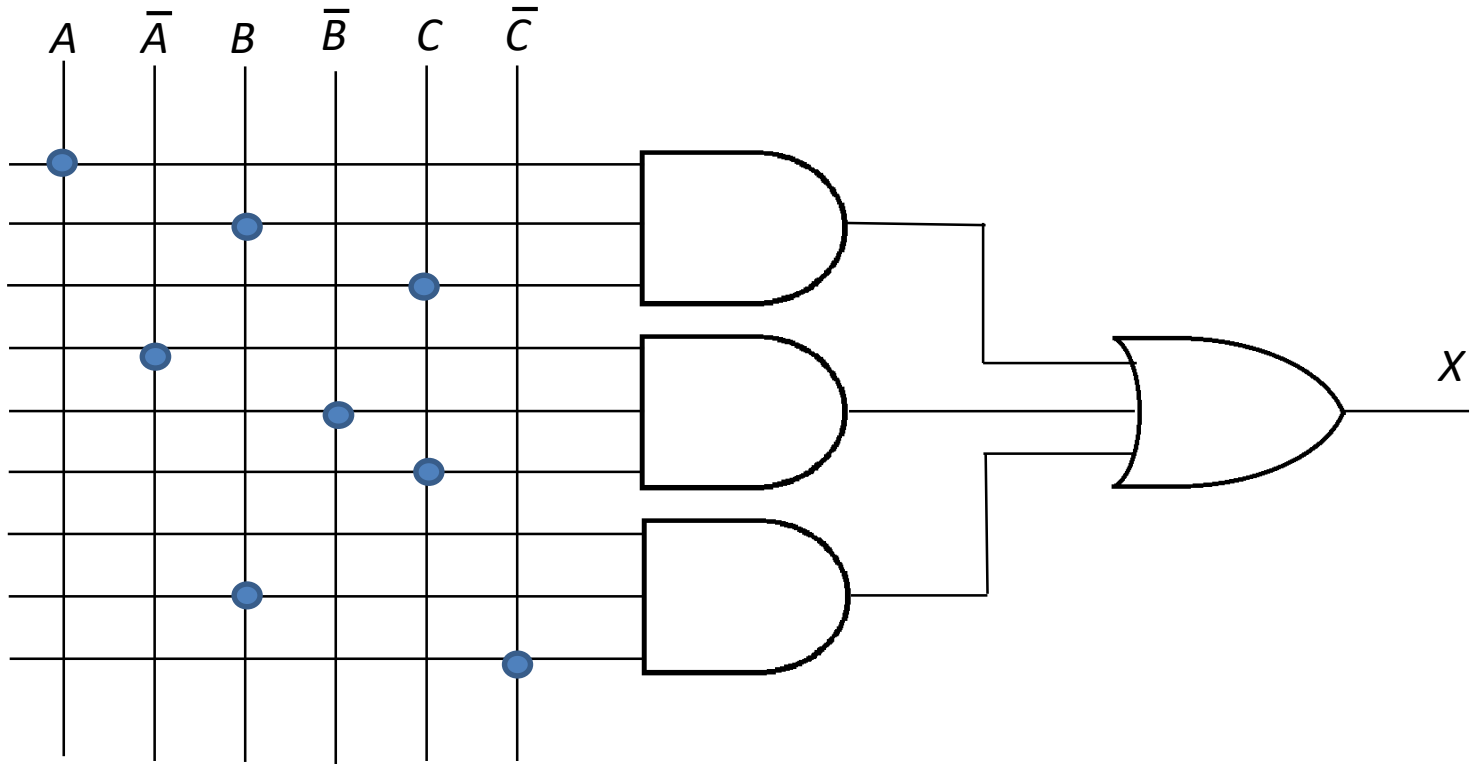

The connections can be “programmed”

Programmable Logic Devices

- LUT (look up table):

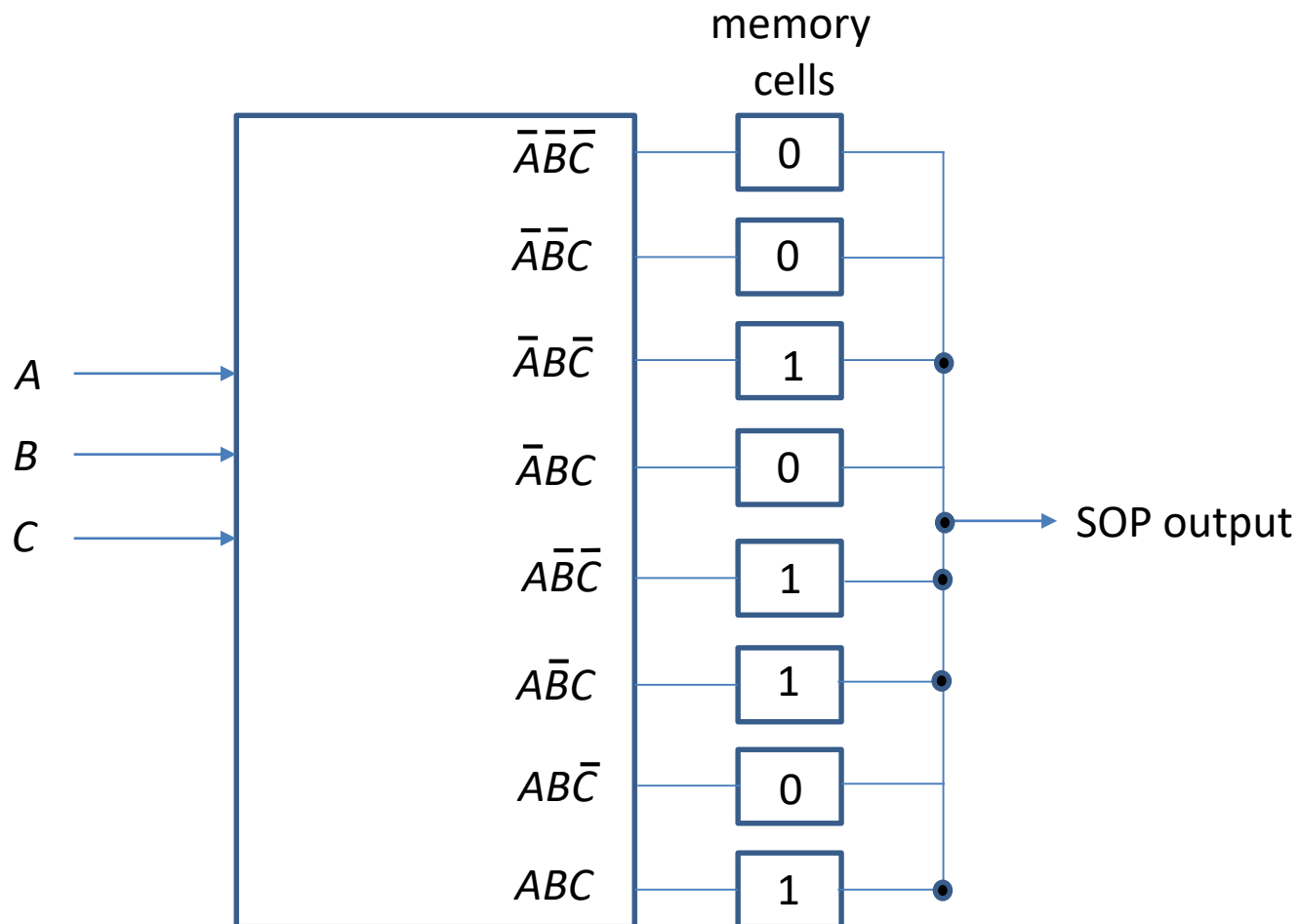


The values in the memory cells are “programmed”

Programmable Logic Devices

- Simple Programmable Logic Devices (SPLD)
- Complex Programmable Logic Devices (CPLD)
 - e.g., with 10-1700 macrocells
 - 10-1156 I/Os
- Field Programmable Gate Array (FPGA)
 - e.g., with 26 to 359,000 CLBs (configurable logic block)
 - each CLB consists of several logic modules
 - 18-1200 I/Os
 - with 50 million gates

Programming FPGA

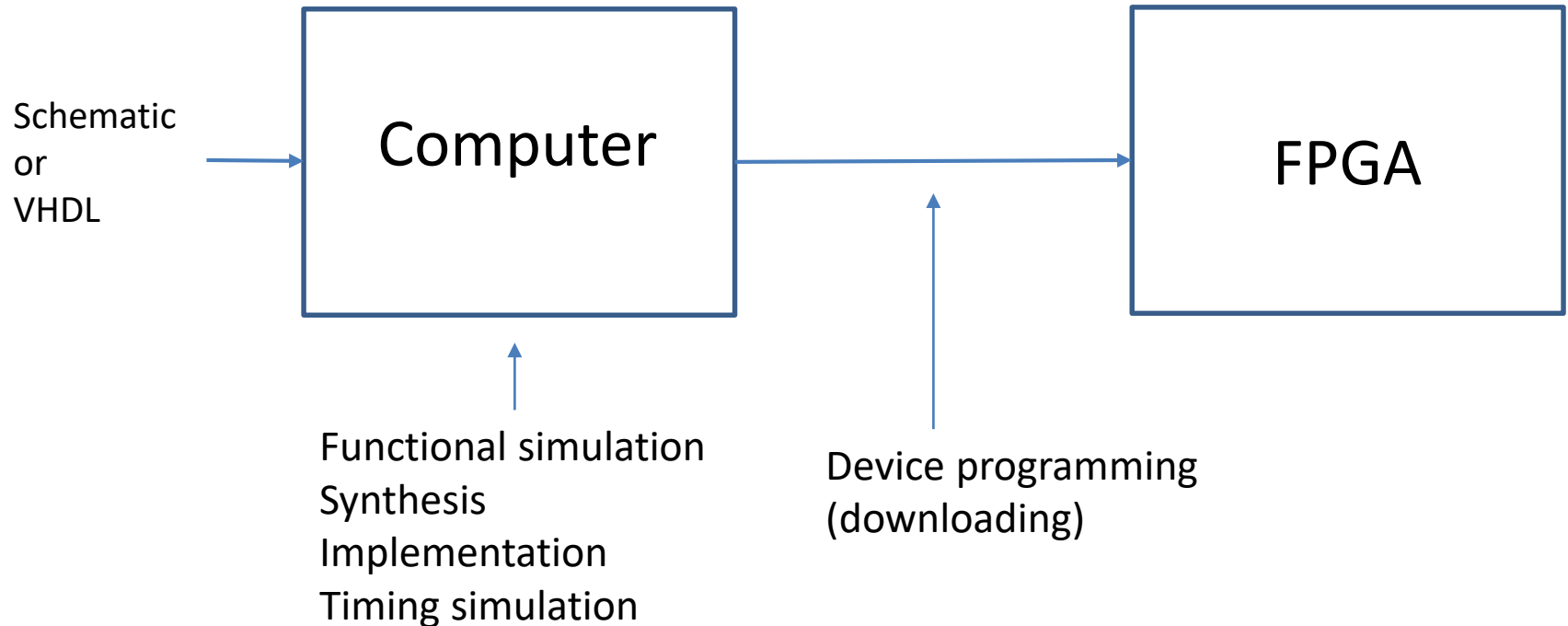

VHDL

- VHDL is a hardware description language

For example, a 7-segment display:

$$X_a = A + C + BD + \bar{B}\bar{D}$$

$$X_b = \bar{B} + CD + \bar{C}\bar{D}$$

VHDL program is

```
entity DisplaySegments is  
    port (A, B, C, D: in bit; Xa, Xb: out bit);  
end entity DisplaySegments  
architecture Expression1 of DisplaySegments is  
begin  
    Xa <= A or C or (B and D) or (not B and not D);  
    Xb <= not B or (C and D) or (not C and not D);  
end architecture Expression1
```